

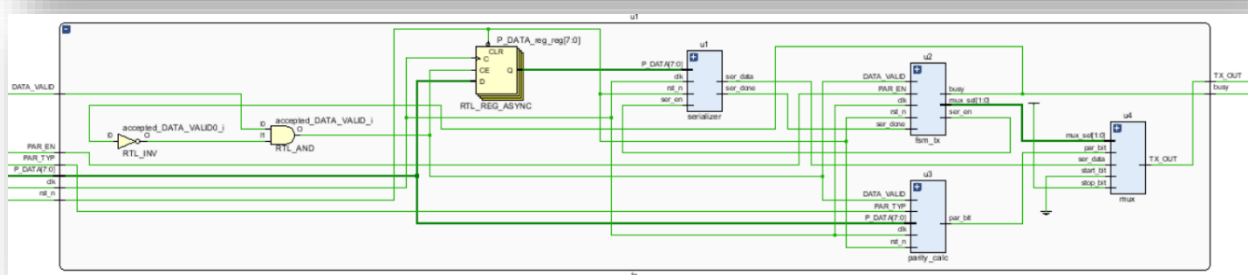


UART



1.TRANSMITTER

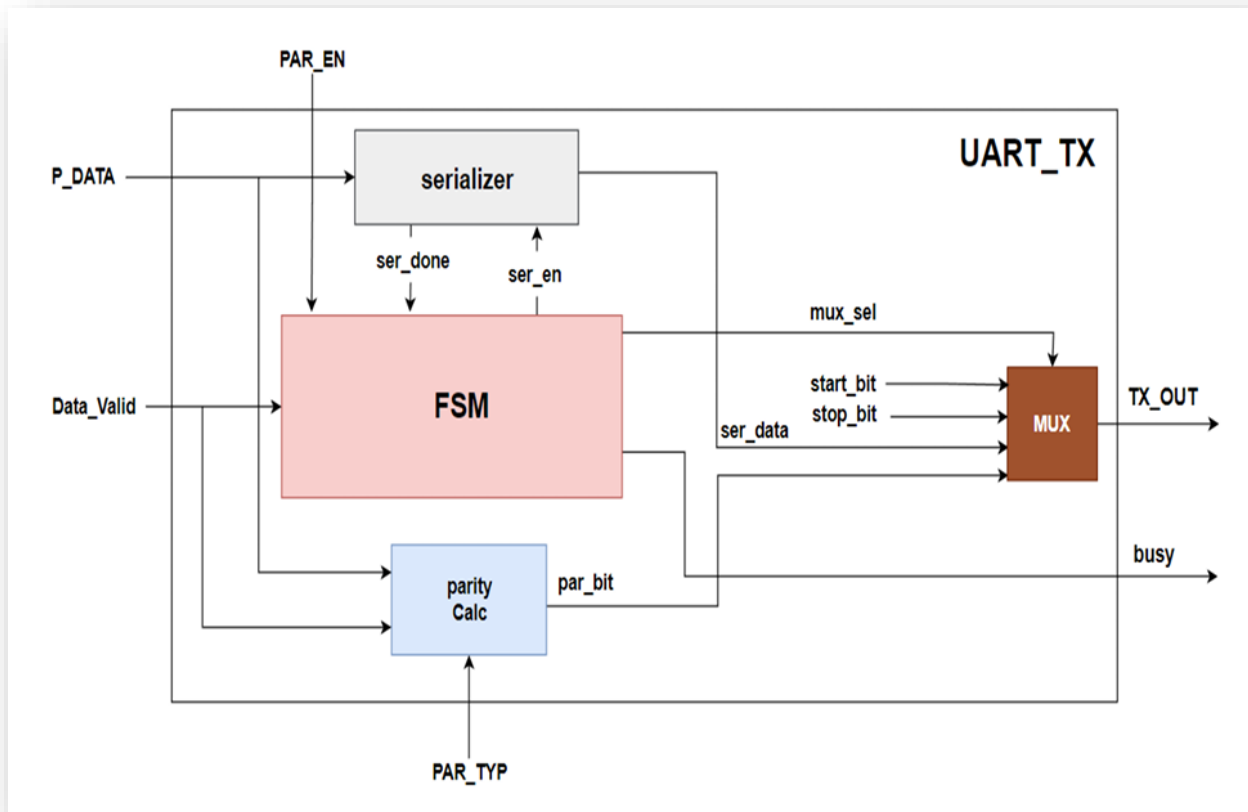


TESTBENCH SIMULATION

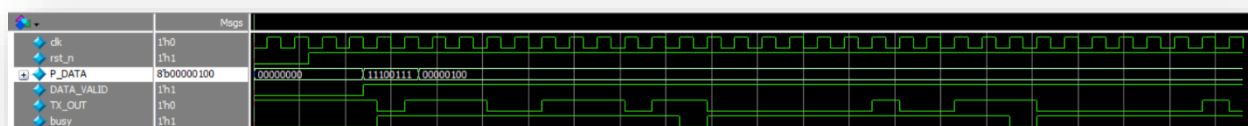


2.RECEIVER

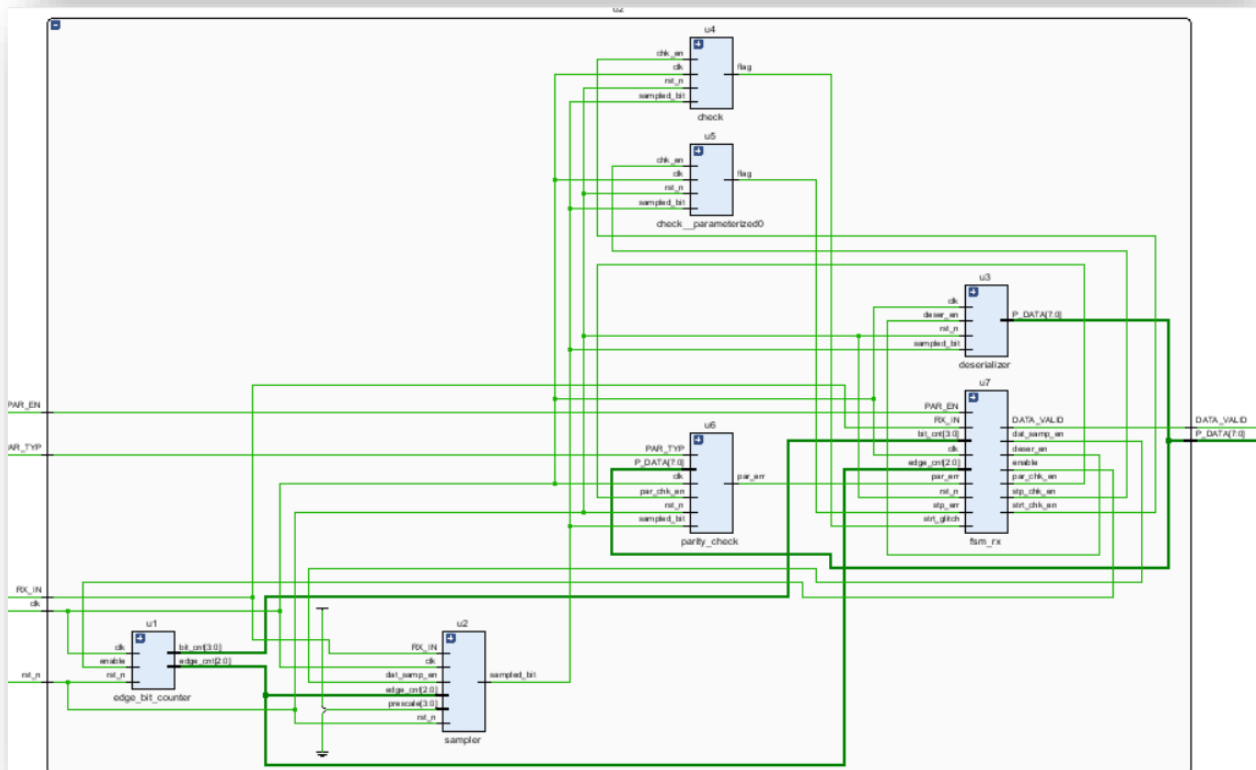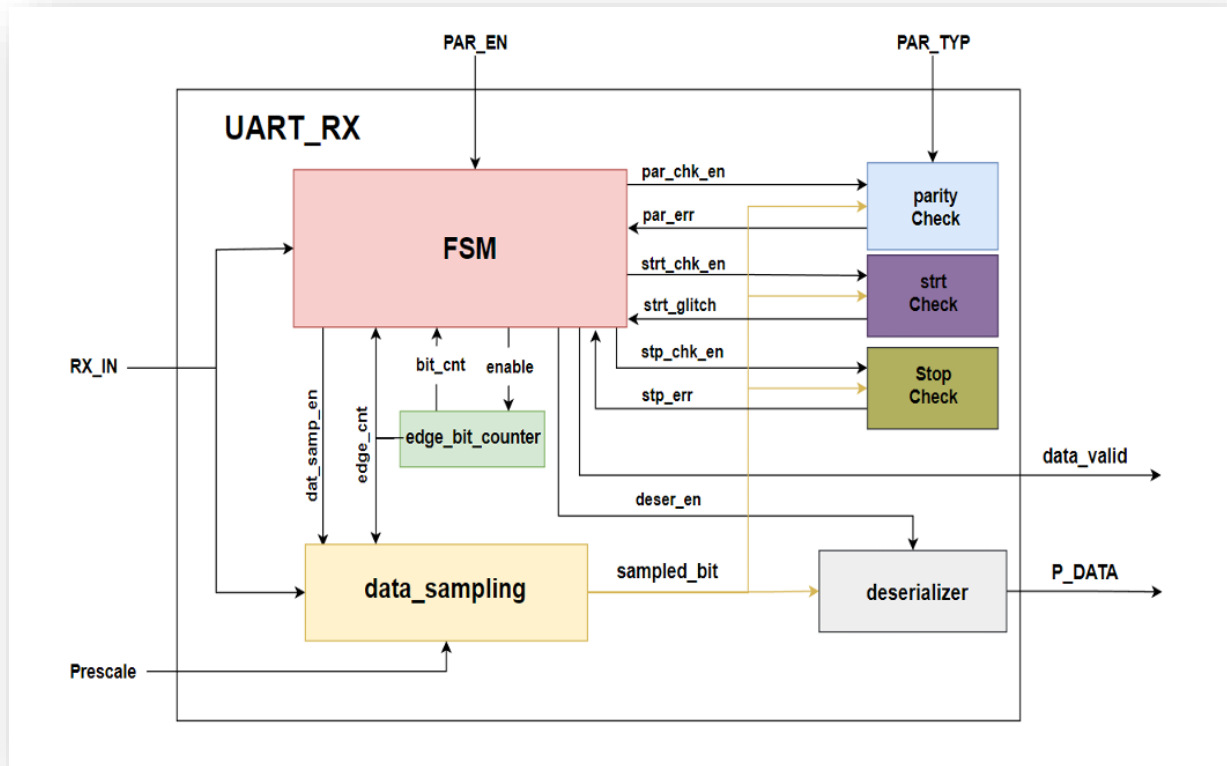

TESTBENCH SIMULATION

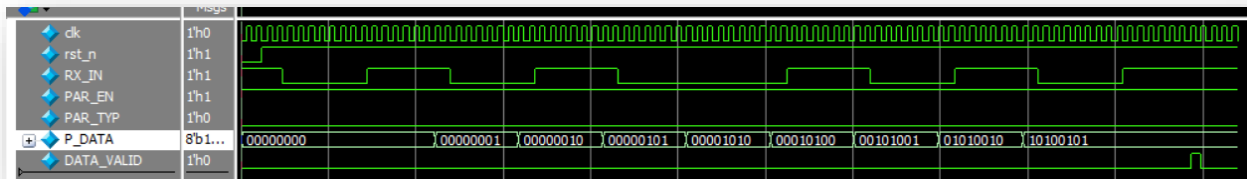

3.UART CONNECTED

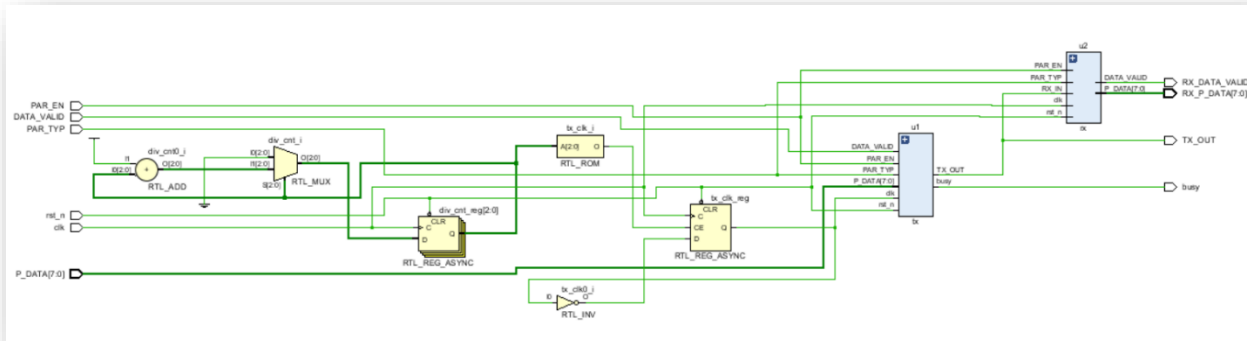

TESTBENCH SIMULATION

